
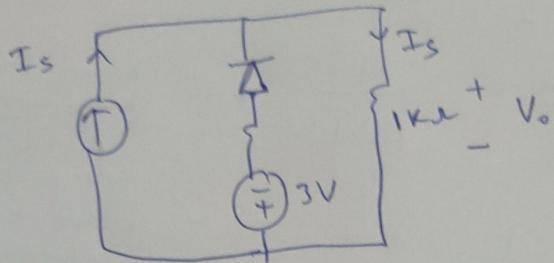


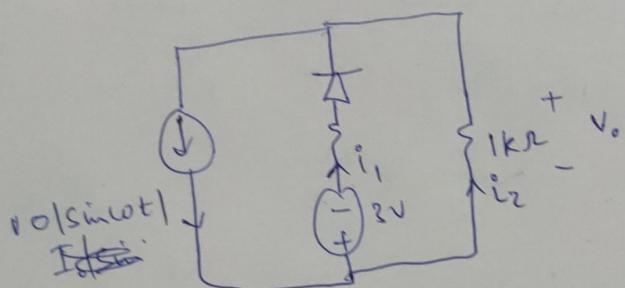Q1 To let  $\frac{2n\pi}{\omega} \leq t \leq \frac{(2n+1)\pi}{\omega}$  where  $n$  is an integer  $> 0$



$$V_o = I_s(1k\Omega) = 10 \sin \omega t \text{ V}$$


$$\text{let } \frac{(2n+1)\pi}{\omega} \leq t \leq \frac{2(n+1)\pi}{\omega}$$



$$\begin{cases} 3 + i_1 = i_2 \\ i_1 + i_2 = 10|\sin \omega t| = -10 \sin \omega t \\ 2i_2 = 3 - 10 \sin \omega t \Rightarrow i_2 = \frac{3 - 10 \sin \omega t}{2} \end{cases}$$

$$V_o = -i_2 = \frac{10 \sin \omega t - 3}{2}$$
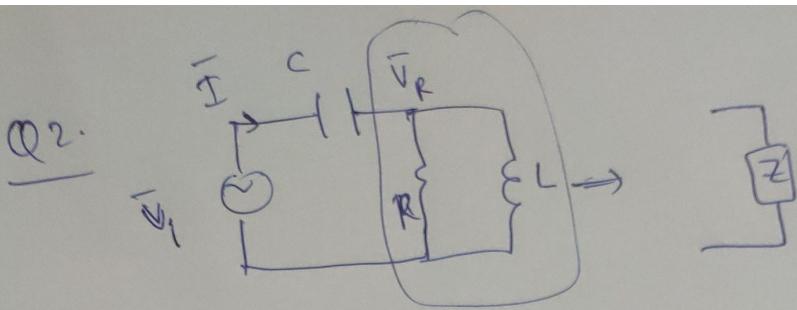
$$\Rightarrow V_o = \begin{cases} 10 \sin \omega t \text{ V} & \frac{2n\pi}{\omega} \leq t \leq \frac{(2n+1)\pi}{\omega} \\ \frac{10 \sin \omega t - 3}{2} \text{ V} & \frac{(2n+1)\pi}{\omega} \leq t \leq \frac{2(n+1)\pi}{\omega} \end{cases}$$



$$Z = R \parallel X_L$$

$$\bar{I} = \frac{\bar{V}_o}{Z + X_C}$$

$$\bar{V}_R = \bar{I} Z$$

$$\Rightarrow \frac{\bar{V}_R}{\bar{V}_i} = H(\omega) = \frac{Z}{Z + X_C}$$

$$= \frac{\frac{RX_L}{R + X_L}}{\frac{RX_C}{R + X_L} + X_C} = \frac{RX_L}{RX_L + RX_C + X_L X_C}$$

$$= \frac{iRL\omega}{iRL\omega - iR\frac{c}{\omega} - \frac{L}{c}} = \frac{-RL\omega}{\frac{R}{c\omega} - RL\omega - i\frac{L}{c}} = \frac{-RLC\omega^2}{R - RLC\omega^2 - iL\omega}$$

$$= \frac{-RLC\omega^2 (R - RLC\omega^2 + iL\omega)}{(R - RLC\omega^2)^2 + L^2\omega^2}$$

$$= \underbrace{\frac{-RLC\omega^2 (R - RLC\omega^2)}{(R - RLC\omega^2)^2 + (L\omega)^2}}_{Re(H(\omega))} + i \underbrace{\left( \frac{-RL^2C\omega}{(R - RLC\omega^2)^2 + L^2\omega^2} \right)}_{Im(H(\omega))}$$

$$H(\omega) = \frac{-RLC\omega^2(R - RLC\omega^2)}{(R - RLC\omega^2)^2 + (L\omega)^2} + i \frac{-RL^2C\omega^3}{(R - RLC\omega^2)^2 + (L\omega)^2}$$

$$\operatorname{Re}(H(\omega)) = 0$$

$$\Rightarrow R = RLC\omega^2$$

$$\boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$$\operatorname{Re}(H(\omega)) = 0 \text{ at } \omega = \frac{1}{\sqrt{LC}}$$

$$\operatorname{Im}(H(\omega)) < 0 \text{ for } \omega$$

$$\Rightarrow \operatorname{Im}(H(\omega)) \rightarrow 0 \text{ as } \omega \rightarrow \infty$$

$$\therefore Q = R \sqrt{\frac{C}{L}} = R \sqrt{\frac{1}{X_L X_C}}$$

$$\Rightarrow R = Q \sqrt{X_L X_C}$$

$$H(\omega) = \frac{X_L}{X_L + X_C + \frac{X_L X_C}{R}} = \frac{X_L}{X_L + X_C + \frac{\sqrt{X_L X_C}}{Q}}$$

~~$$\frac{X_L}{X_L + X_C}$$~~

~~as  $\omega \rightarrow \infty$~~

$$H(\omega) \approx \frac{X_L}{X_L + X_C} = \frac{i\omega}{i\omega + \frac{1}{C\omega}} \quad \text{or} \quad (iv)$$

$$H(\omega) = \frac{X_L}{X_L + X_C}$$

$$H(\omega) = \frac{\left( \frac{X_L}{X_L + X_C} \right)}{1 + \left( \frac{\sqrt{X_L X_C}}{X_L + X_C} \right) \frac{1}{Q}}$$

$\ll 1$



$$= \left( \frac{X_L}{X_L + X_C} \right) \left( 1 - \frac{\sqrt{X_L X_C}}{X_L + X_C} \frac{1}{Q} \right)$$

$$= \left( \frac{X_L}{X_L + X_C} - \frac{X_L \sqrt{X_L X_C}}{(X_L + X_C)^2} \frac{\sqrt{X_L X_C}}{R} \right)$$

$$= \frac{X_L}{X_L + X_C} - \frac{X_L^2 X_C}{R(X_L + X_C)^2}$$

$$= \frac{iL\omega}{iL\omega + i\frac{1}{C\omega}} - \frac{i \left( \frac{L^2 \omega^2}{C\omega} \right)}{-R \left( L\omega - \frac{1}{C\omega} \right)^2}$$
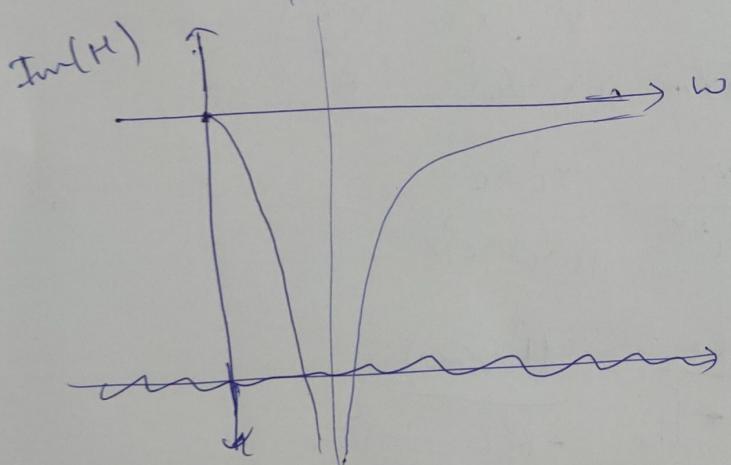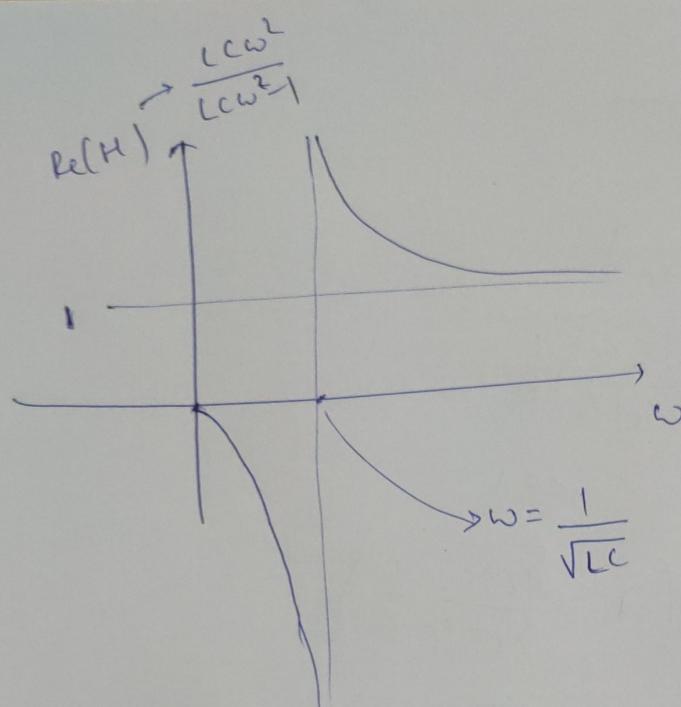
$$= \underbrace{\frac{LC\omega^2}{LC\omega^2 - 1}}_{Re} + \underbrace{i \left( \frac{-L^2 C \omega^3}{R(LC\omega^2 - 1)^2} \right)}_{Im}$$




$$H(\omega) = \frac{LC\omega^2}{(LC\omega^2 - 1)} \left[ 1 + i \frac{-i\omega}{R(LC\omega^2 - 1)} \right]$$


$$\left| H(\omega) \right|_{\max} = H(\omega) = \frac{X_L}{X_L + X_C} \left( 1 - \frac{\sqrt{X_L X_C}}{X_L + X_C} \frac{1}{\alpha} \right)$$

$$\boxed{\left| H(\omega) \right|_{\max} \approx \frac{X_L}{X_L + X_C} = \frac{LC\omega^2}{LC\omega^2 - 1}}$$

Q3. for  $t < 0$

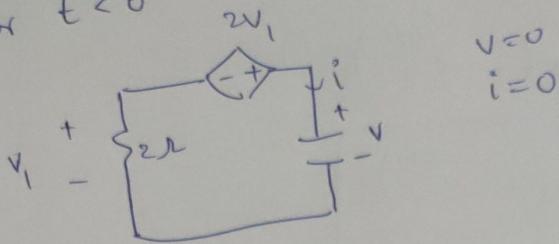

for  $t > 0$  (let  $t$  at time  $t$ )

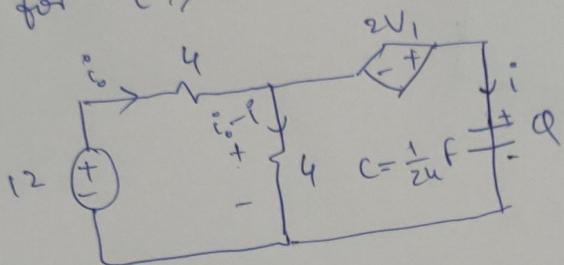

$$i_2 = 4i_0 + 4i - 4i = 8i_0 - 4i$$

$$v_1 = 4i_0 - 4i$$

$$i_2 = -8i_0 + 8i + \frac{Q}{C}$$

$$2u = 4i + \frac{dQ}{dt}$$

$$\cancel{i = \frac{dQ}{dt}}$$

$$4 \frac{dQ}{dt} = 2u - \frac{Q}{C}$$

$$\int_0^Q \frac{dQ}{2u - Q/C} = \int_0^t \frac{dt}{4}$$

$$\left( \ln(2u - Q/C) \right)_0^Q = -\frac{t}{4C}$$

$$2u - Q/C = 2u e^{-t/4C}$$

$$\Rightarrow Q = 2u C \left( 1 - e^{-t/4C} \right)$$

$$V(t) = \frac{Q}{C} = 2u(1 - e^{-\frac{t}{6}})$$


$$V(t) = 2u(1 - e^{-6t})$$

$$i(t) = \frac{dQ}{dt} = 6e^{-6t}$$

$$\Rightarrow V(t) = \begin{cases} 0 & t < 0 \\ 2u(1 - e^{-6t}) & t \geq 0 \end{cases}$$

$$i(t) = \begin{cases} 0 & t < 0 \\ 6e^{-6t} & t \geq 0 \end{cases}$$

Q4.

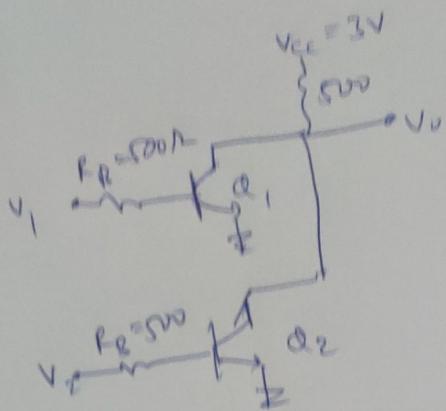

i)  $V_1 = V_2 = 0\text{V}$

Assume  $Q_1, Q_2 \rightarrow$  cut off

$$V_C = V_{C2} = V_{CC} = 3V = V_0$$

$$V_{BE1} = V_{BE2} = 0.2 < 0.5$$

Assumption correct.

ii)  $V_1 = 3V, V_2 = 0.2V$

Assume  $Q_2 \rightarrow$  cut off,  $Q_1 \rightarrow$  sat

$$V_B = 0.8V \quad i_B = \frac{6.2}{500} = 0.0124mA$$

$$V_{B1} = 0.8V \rightarrow i_{B1} = \frac{2.2}{500} A$$

$$V_{C1} = \boxed{V_0 = 0.2V}$$

$$i_{C1} = \frac{(3 - 0.2) \times 2}{500} = \frac{2.8 \times 2}{500}$$

$$\frac{i_{C1}}{i_{B1}} \epsilon < \beta \quad \epsilon \quad V_{BE} = 0.2 < 0.5$$

Assumption correct

$$(iii) V_1 = 0.2V \quad V_1 = \frac{3}{4}V$$

same as (ii)

$$(iv) V_1 = 3V = V_2$$

Assume Q<sub>1</sub>, Q<sub>2</sub> sat

$$V_{B1} = V_{B2} = 0.8 \quad i_{B1} = i_{B2} = \cancel{0.1} \frac{2.2}{500}$$

$$\boxed{V_{C1} = V_{C2} = 0.2V = V_g}$$

$$i_{C1} = i_{C2} = \cancel{0.1} \frac{2.8}{500}$$

$$\frac{i_{C1}}{i_{B1}} = \frac{i_{C2}}{i_{B2}} < B \quad \text{if } V_g \cancel{\text{is}}$$

Assumption correct.

NOR GATE

Q5.

$$V_T(M_1, M_2) = 1V$$

$$V_T(M_3, M_4) = -1V$$

$$k = 0.25 \text{ mA/V}^2$$

Assume  $M_1$  &  $M_2$  is active region

$$V_{AS4} = V_2 - V_{DD} = 0$$

So  $M_4$  is off (as  $V_{AS}$  should be  $< 0$  for it to be ON)

Assume  $M_3$  to be in ohmic region.

as  $M_4$  is off  $i_{D4} = 0$  so,

$$i_{D3} = i_{D2} = i_{D1}$$

$$\cancel{i_{DS}} = k [2(V_{AS1} - V_T)]$$

$$i_{D1} = k (V_{AS1} - V_T)^2$$

$$V_{AS1} = V_1 = 4V$$

$$\Rightarrow i_{D1} = k (3)^2 = 9k$$

$$i_{D2} = k (V_{AS2} - V_T)^2$$

$$V_{AS2} = V_2 - V_{DS1} = 10 - V_{DS1}$$

$$\rightarrow i_{D2} = k (9 - V_{DS1})^2 = i_{D1}$$

$$K(a - V_{DS1})^2 = K(3)^2$$

$$\Rightarrow \boxed{V_{DS1} = 6 \text{ V}}$$

$$V_{AS3} = V_i - V_{DD} = 4 - 10 = -6 \text{ V}$$

$$\therefore i_{D3} = K \left[ 2(V_{AS3} - V_T) V_{DS3} - V_{DS3}^2 \right]$$

$$\Rightarrow qK = K \left[ -10V_{DS3} - V_{DS3}^2 \right]$$

$$\Rightarrow V_{DS3}^2 + 10V_{DS3} + 9 = 0$$

$$V_{DS3} = -\frac{10 \pm 8}{2} = -1, -9$$

$$\text{let } V_{DS3} = -9$$

$$V_{AS3} - V_T = -6 + 1 = -5$$

$$V_{DS3} < V_{AS3} - V_T \quad (\text{contradiction})$$

so discard  $V_{DS3} = -9$

$$\text{let } V_{DS3} = -1$$

$$H_2(V_{DS3} = -1) > (V_{AS3} - V_T = -5)$$

So our assumption is correct.

$M_3$  is indeed in ohmic mode

$$V_{DS3} = V_o - V_{DD}$$

$$\Rightarrow V_o = 10 - 1 = 9V$$

$$(V_{DS1} = 6V) > (V_{GS1} - V_T = 3V)$$

So  $M_1$  is indeed in active region


$$V_{DS2} = V_o - V_{DS1} = 9 - 6 = 3V$$

$$(V_{DS2} = 3V) > (V_{GS2} - V_T = 3V)$$

So  $M_2$  is indeed in active region

Q6.

Assume virtual short (ie  $v_+ = v_-$ )

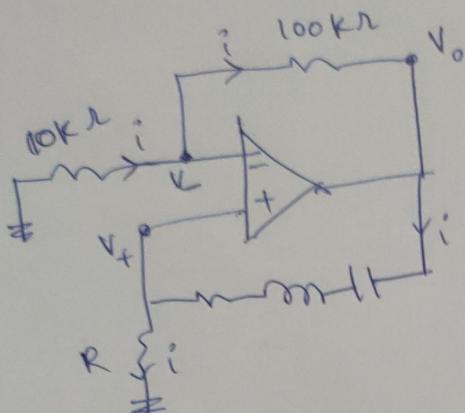

$$v_- = v_+$$

$$i = \frac{v_-}{10} = \frac{v_o - v_-}{100} \Rightarrow v_o = 11v_-$$

~~$$i = \frac{v_+}{R} = \frac{v_o - v_+}{12\text{eqv}} \Rightarrow 10R = 12\text{eqv}$$~~

$$(10R)^2 = 5^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \times 10^{-6}$$


~~or~~

$$\Rightarrow 10R > 5 \Rightarrow f > 0.5 \text{ kHz}$$

for ~~R=500Ω~~,  $\omega = \frac{1}{\sqrt{LC}}$

$$= \frac{1}{\sqrt{0.2 \times 10^{-3} \times 5 \times 10^{-9}}} = 10^6 \text{ rad/s}$$

Q7.

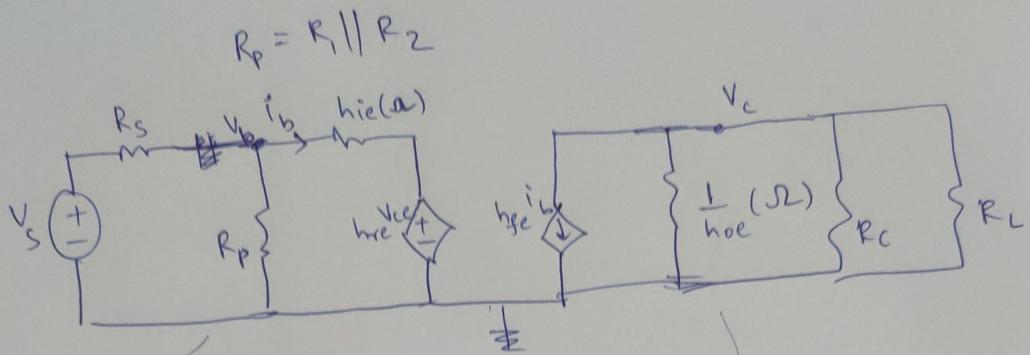

$$\frac{V_s - V_b}{R_s} = \frac{V_b}{R_p} + i_b$$

$$i_b = \frac{V_s - V_b}{R_s} - \frac{V_b}{R_p}$$

$$i_b h_{ie} + h_{re} V_c = V_b \quad \text{*}$$

$$V_c = -h_{fe} i_b \left( \frac{1}{h_{re}} \parallel R_C \parallel R_L \right)$$

$$\Rightarrow V_c = -h_{fe} i_b R_X$$

$$\rightarrow \left( \frac{V_s - V_b}{R_s} - \frac{V_b}{R_p} \right) h_{ie} + h_{re} (-h_{fe} i_b R_X) = V_b$$

$$\rightarrow i_b h_{ie} + h_{re} (-h_{fe} i_b R_X) = V_b$$

$$\Rightarrow V_b = i_b (h_{ie} - h_{re} h_{fe} R_X)$$

$$\therefore V_c = i_b (-h_{fe} R_X)$$

$$\Rightarrow \frac{V_c}{V_b} = \frac{i_b(-h_{fe}R_x)}{i_d(h_{ie} - h_{re}h_{fe}R_x)}$$

$$= \frac{h_{fe}R_x}{h_{re}h_{fe}R_x - h_{ie}}$$



$$R_x = R_e \frac{1}{h_{oe}} \parallel R_c \parallel R_L = 100 \parallel 12 \parallel 2 = 100 \parallel 1$$

$$R_x = \frac{100}{101}$$

$$\text{Voltage gain} = \frac{100 \left( \frac{100}{101} \right)}{\left( 10^{-2} \right) \left( \frac{100}{101} \right) - 1 \cdot 3} = \frac{\cancel{\left( \frac{10^4}{101} \right)}}{\cancel{\left( \frac{10^4}{101} \right)} - 1 \cdot 3} \rightarrow$$

$$= \frac{10^4}{1 - 1.3(101)} = - \frac{10^4}{130.3} = -76.745$$
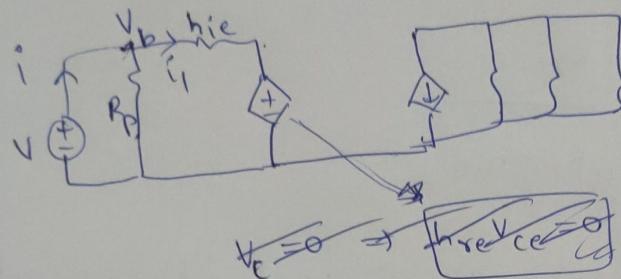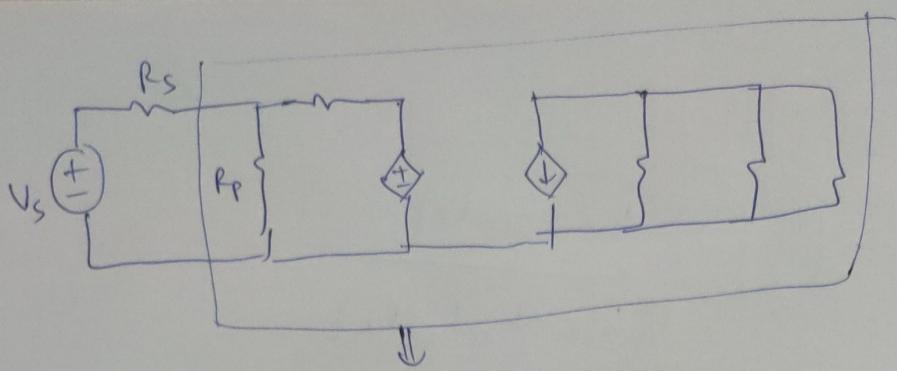
$$\therefore \text{Voltage gain} = -76.745 \quad (\text{A})$$



$$i = \frac{V_b}{R_p} + \frac{h_{re}}{h_{ie}} i_1$$

$$V = V_b$$

$$i_1 h_{ie} + h_{re} V_c = V$$

$$i_1 h_{ie} + h_{re} A_v V_E = V$$

$$i_1 = \frac{V(1 - h_{re} A_v)}{h_{ie}}$$

$$i = \frac{V}{R_p} + \frac{V(1 - h_{re} A_v)}{h_{ie}}$$

$$\frac{V}{i} = \frac{1}{\frac{1}{R_p} + \left( \frac{1 - h_{re} A_v}{h_{ie}} \right)} = R_{in}$$

$$R_p = R_1 \parallel R_2 = 10 \text{ k}\Omega$$

$$\Rightarrow R_{in} = \frac{1}{\frac{1}{10} + \left( \frac{1 + 10^4 (A_v)}{h_{ie}} \right)} = 1.1426 \text{ k}\Omega$$

# PDF Created Using



## Camera Scanner

Easily Scan documents & Generate PDF



<https://play.google.com/store/apps/details?id=photo.pdf.maker>